

JNTU Kakinada

MODEL QUESTION PAPER (R23 PATTERN)

Model Question Paper 1 ? Digital Logic Design (Latest Pattern)

Subject Code: CS302 Semester: 3 Regulation: R23

Time: 3 Hours Max. Marks: 70

.....
Note: This is a demo question paper generated for Backlog Buddy.

Answer all questions. Assume suitable data wherever necessary.
.....

SECTION A (Unit 1: Number Systems and Codes)

1. Describe the working principle of Number Systems and Codes with necessary equations. [12 Marks]
2. Solve a problem related to Number Systems and Codes. Show all the steps clearly. [8 Marks]
3. List the advantages and limitations of Number Systems and Codes. Explain any two in detail. [12 Marks]

SECTION B (Unit 2: Boolean Algebra and K-Maps)

4. Explain Boolean Algebra and K-Maps with a neat diagram/sketch and a suitable example. [8 Marks]
5. List the advantages and limitations of Boolean Algebra and K-Maps. Explain any two in detail. [12 Marks]
6. Write short notes on Boolean Algebra and K-Maps. [12 Marks]

SECTION C (Unit 3: Combinational Circuits)

7. Explain Combinational Circuits with a neat diagram/sketch and a suitable example. [12 Marks]
8. Define Combinational Circuits. Explain its significance in Digital Logic Design with a suitable example. [8 Marks]
9. Compare and contrast the key concepts involved in Combinational Circuits. [12 Marks]

SECTION D (Unit 4: Sequential Circuits)

10. Define Sequential Circuits. Explain its significance in Digital Logic Design with a suitable example. [12 Marks]
11. Derive the expression related to Sequential Circuits and explain each term. [12 Marks]
12. Write short notes on Sequential Circuits. [12 Marks]

SECTION E (Unit 5: Memory and Programmable Logic)

13. Describe the working principle of Memory and Programmable Logic with necessary equations. [12 Marks]

14. Solve a problem related to Memory and Programmable Logic. Show all the steps clearly. [12 Marks]

15. Define Memory and Programmable Logic. Explain its significance in Digital Logic Design with a suitable example. [12 Marks]

*** End of Question Paper ***